



- 1) Compute the total power consumption.
- 2) Model the circuit in PhET (lab section has kilo-Ohm resistors).
- 3) Compare results.