

# Wednesday Reading Assessment: Unit 1, Ohm's Law, Resistors in Complex Circuits

Prof. Jordan C. Hanson

February 14, 2024

## 1 Memory Bank

- $V = IR$  ... Ohm's Law, with  $V$  for voltage,  $I$  for current, and  $R$  for resistance.
- $R_{tot} = R_1 + R_2$  ... Total resistance of two resistors in series.
- $R_{tot}^{-1} = R_1^{-1} + R_2^{-1}$  ... Total resistance of two resistors in parallel.
- $P = IV$  ... The power consumed by a device that draws a current  $I$  at a voltage  $V$ .
- $I = \Delta Q / \Delta t$  ... The definition of current, a change in charge versus time.

## 2 Current from Resistance and Voltage

1. (a) Suppose an electrical circuit is comprised of a 5V battery, and two  $1\text{k}\Omega$  resistors *in series*. What is the current flowing from the battery? (b) Suppose an electrical circuit is comprised of a 5V battery, and two  $1\text{k}\Omega$  resistors *in parallel*. What is the current flowing from the battery?

## 3 Power

1. (a) Compute the power consumption for the circuits in parts (a) and (b) of the previous problem. (b) If the battery has 10 A hr of charge, how long will the battery last in each case?