

Tuesday Reading Assessment: Unit 4, Reactance and Impedance

Prof. Jordan C. Hanson

April 8, 2024

1 Memory Bank

- $X_C = 1/(2\pi fC)$... The reactance of a capacitor with capacitance C , at frequency f .
- $X_L = 2\pi fL$... The reactance of an inductor with inductance L , at frequency f .
- $Z_{\text{tot}} = \sqrt{R^2 + (X_L - X_C)^2}$... The total impedance of a series circuit with resistance R , and reactances X_C and X_L .
- $\tau = RC$... The time constant of an RC circuit.
- $f_0 = \frac{1}{2\pi\sqrt{LC}}$... The resonance frequency of an RLC circuit.

2 Reactance, Impedance, and Waveforms

1. (a) What is the reactance of a capacitor with $C = 0.1 \mu\text{F}$ at a frequency $f = 1 \text{ MHz}$? (b) What will the reactance be at $f = 0.5 \text{ MHz}$? (c) If this capacitor is installed in an RC circuit with a 50Ω resistor, what is the total impedance? (d) What is the time constant of this circuit?
2. (a) What is the total impedance of an RLC circuit at $f = 10 \text{ kHz}$, if $R = 100 \Omega$, and $C = 10 \text{ pF}$, and $L = 1 \mu\text{H}$? (b) What is the resonance frequency of this circuit?
3. An amplitude modulated radio wave is generated by a mixer based on an LC resonating circuit (see Fig. 1). The carrier, with frequency f_C , and the audio, with frequency f_A , are *mixed*. The modulated result is comprised of two frequencies: $f_C - f_A$, and $f_C + f_A$. (a) If we have an audio signal at 4 kHz and a carrier at 1 MHz , what are the final frequencies? (b) Given what you know about *filtering*, how would you construct a circuit that only responds to the signal at $f_C + f_A$?

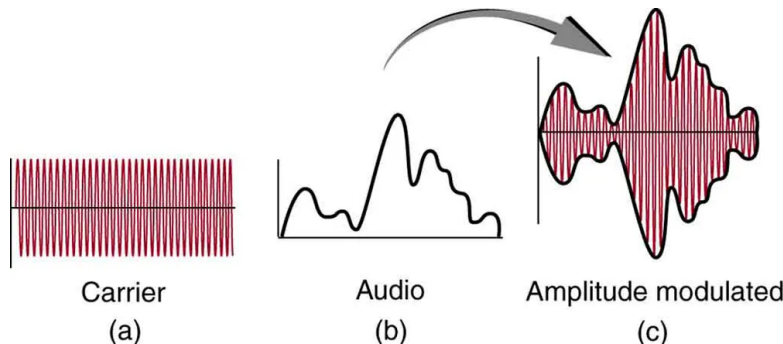


Figure 1: An example of an amplitude modulated (AM) waveform.