

Midterm 2

2.1. a) $\tau = RC$

Problem states RC time constant must be less than 100, so:

$$100 \mu s \left(\frac{1.0 \times 10^{-6} s}{1 \mu s} \right) > 1 k\Omega \left(\frac{1 \times 10^3 \Omega}{1 k\Omega} \right)$$

$$1 \times 10^{-4} s > 1 \times 10^3 \Omega (C)$$

$$C < \frac{1 \times 10^{-4} s}{1 \times 10^3 \Omega}$$

$$C < 1 \times 10^{-7} F$$

b) It would not be difficult, just use a capacitor with less capacitance.

c) $V = V_0 (1 - e^{-t/\tau})$

$$30 = 60 (1 - e^{-(\frac{t}{100 \times 10^{-6}})})$$

$$\frac{1}{2} = e^{-(\frac{t}{100 \times 10^{-6}})}$$

$$t = 6.9 \times 10^{-5} \text{ seconds}$$

2.2. a) $V(t) = V_0 \sin(2\pi f t + \phi)$

 $\therefore 0$ is also equal to $\sin(\pi)$

$$0 = 120 V \sin(2\pi(60 \text{ Hz})t + 0)$$

$$\sin(2\pi(60 \text{ Hz})t) = 0$$

$$\sin(2\pi(60 \text{ Hz})t) = \pi$$

$$t = \frac{\pi}{2\pi(60 \text{ Hz})}$$

$$t = 8.33 \times 10^{-3} \text{ seconds}$$

b) $\text{Power}_{\text{max}} = V_{\text{max}} (I_{\text{max}})$

$$\therefore I = \frac{V}{R}$$

$$P_{\text{max}} = V_{\text{max}} \left(\frac{V}{R} \right)$$

$$P_{\text{max}} = V_{\text{max}}^2 \left(\frac{1}{R} \right)$$

$$P_{\text{max}} = \frac{1}{10^3 \Omega} (120 V)^2$$

$$R = 1 k\Omega, V_{\text{max}} = 120 V$$

$$P = \frac{V^2}{R}$$

$$P_{\text{max}} = 14.4 W$$

c) $P = \frac{V^2}{R}$

$$\text{Avg power} = \frac{1}{2} \frac{V^2}{R} = \frac{1}{2} (14.4 W)$$

$$\text{Avg. Power} = 7.2 W$$

2.3) $P = VI$

$P = 110V(3A) = 330W$

Total watts = $330W + 60W + 100W + 3W = 493W/hr$

Per day: $493W/hr (12hrs) = 5916W$

$= 5.92 \text{ Kwatt} \cdot hr$

If a kwatt hour costs 0.2 dollars

$\rightarrow 5.916 \text{ Kwatt} \cdot hr (0.2 \text{ dollars})$

$= 1.1832 \text{ dollars a day}$

Per month = $1.1832 (30 \text{ days})$

$= \$35.50$

3.1) $i_2 + i_3 = i_1$ (Junction rule)

$1 \text{ k}\Omega = 1000\Omega$

$V = IR$

$I = \frac{V}{R}$

$12 = I_3 R$

$I_3 = \frac{12V}{1 \text{ k}\Omega} = 0.012A = 12mA$


$I_2 = \frac{12V}{1 \text{ k}\Omega} = 0.012A = 12mA$

$I_1 = 12mA + 12mA = 24mA$ (Junction rule)

$P = I^2 R$

$\left(\frac{12}{1000}\right)^2 1 \text{ k}\Omega + \left(\frac{24}{1000}\right)^2 1 \text{ k}\Omega + \left(\frac{12}{1000}\right)^2 1 \text{ k}\Omega$ $1 \text{ k}\Omega = 1000\Omega$

0.864 W

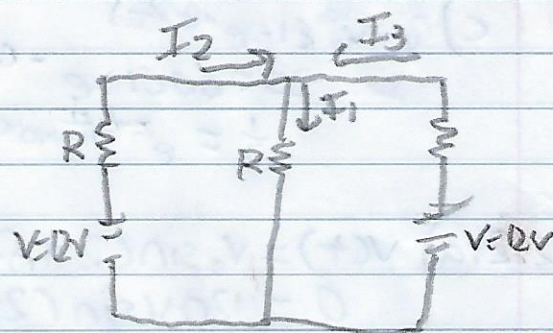


$\frac{1}{R_{eq}} = \frac{1}{2 \text{ k}\Omega} + \frac{1}{2 \text{ k}\Omega} = \frac{2}{2 \text{ k}\Omega} = \frac{1}{1 \text{ k}\Omega}$

and by the junction rule (Voss) $i_1 = i_2 + i_3$

Power consumed Since $1W = 1VA$

$\sigma = V^2/R = 96 \text{ mW} = 0.096 \text{ W}$

$= 0.096 \text{ W}$

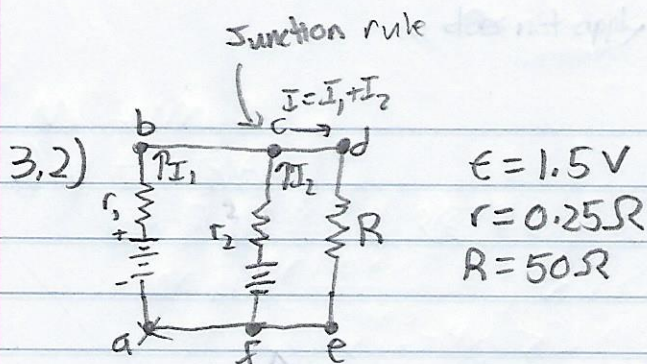

$$B) I = \frac{2q}{t}$$

$$It = 2q$$

$$t = \frac{2q}{I}$$

$$t = \frac{2(2.5A \cdot hr)}{0.030}$$

$$t = 166.7 \text{ hours}$$

a) Loop rule $I = I_1 + I_2$

$$\textcircled{1} E_1 - i_1 r_1 - IR = 0$$

$$\textcircled{2} E_2 - i_2 r_2 - IR = 0$$

$$\therefore i_1 = i_2$$

$$E_1 - i_1 r_1 - IR = E_2 - i_2 r_2 - IR$$

$$E_1 - E_2 - i_1 r_1 + i_2 r_2 = 0$$

$$0.25i_1 - 0.25i_2 + 1.5V - 1.5V = 0$$

$$i_2 r_2 + (i_1 + i_2)R - E_2 = 0$$

$$0.25i_2 + (2i_2)(50) - 1.5V = 0$$

$$i_2 = 0.015A$$

$$\text{Since } i_2 = i_1, \text{ total flow is } i_1 + i_2 = 0.015A + 0.015A = 0.030A$$

4.1) a) Left hand rule: magnetic field is into page

Charge is positive

b) The particle is positively charged, but has the mass of an electron. This is strange because you would expect the sub-atomic particle to have the mass of a proton due to the positive charge.

c) Lorentz force $q = 1.6 \times 10^{-19}C$

$$\vec{F} = q\vec{v} \times \vec{B}$$

$$\vec{F} = (1.6 \times 10^{-19}C)(10^6 m/s)(0.05T)$$

$$\vec{F} = 8 \times 10^{-15}N \text{ to the left}$$