

# Physics Midterm 2 Tanner Barnes

#1.) a.  $R = 1 \text{ k}\Omega = 10^3 \Omega$  time =  $100 \times 10^{-6} \text{ s}$

$\tau = RC$

$C = \frac{100 \times 10^{-6}}{10^3} \text{ F} = 100 \text{ nF}$

b. No, it is not desirable to make a capacitor with capacitance less than  $100 \text{ nF}$

c.  $R = 10^3 \Omega$   $V_0 = 60 \text{ mV}$   
 $V = 30 \text{ mV}$

$V = V_0 (1 - e^{-t/RC})$

$30 = 60 (1 - e^{-t/100 \times 10^{-6}})$

$0.5 = e^{-t/100 \times 10^{-6}}$

$0.693 = \frac{t}{100 \times 10^{-6}}$

$t = 6.93 \times 10^{-5} \text{ seconds}$

#2) a.  $\Phi = 0$   $V(t) = V_0 \sin(2\pi ft)$

$V(t) = 0$  when  $\sin(2\pi ft) = 0$

$2\pi ft = n\pi$

$V(t) = 0$  when  $t = \pm \frac{n}{2f}$  for  $n = 0, 1, 2, \dots$

Because sin function will hit 0 over & over.

b.)  $P_{\max} = \frac{V_{\max}^2}{4R_L} = \frac{(120)^2}{4 \times 1000} = 14.4 \text{ W to } 1 \text{ k}\Omega \text{ Resistor}$

c.) Since it's alternating between 0 + a max of  $14.4 \text{ W}$ , the average would be  $7.2 \text{ W}$  delivered to the resistor

### #3 Power of Refrigerator

$$U = 110 \text{ Volts} \times I = 3 \text{ A} = 330 \text{ Watts}$$

$$\text{Lamp} = 100 \text{ W}$$

$$\text{Overhead Lights} = 50 \text{ W}$$

$$\text{All other} = 3 \text{ W}$$

$$\text{total power consumed} = 493 \text{ Watts}$$

$$\text{Per Day} = 12 \times 493 = 5916 \text{ watt hours} = 5.916 \text{ kwatt hr.}$$

$$\text{kwatt cost } 0.2 \text{ dollars } \underbrace{\text{day}} \quad \underbrace{\text{month}}$$

$$0.2 \times 5.916 \times 30 = 35.496 \text{ dollars}$$

$$\approx \$35.50$$

### # 3.1 Left Hand Side (LHS)

$$U - i_2 R - i_1 R = 0$$

(RHS)

$$R_{\text{eq}} \text{ (parallel)} \quad \frac{R_1 \times R_2}{R_1 + R_2} = \frac{2R \times 2R}{2R + 2R} = R$$

$$U - i_3 R - i_1 R = 0$$

$$\text{Junction Rule } i_1 = i_2 + i_3$$

$$U - i_2 R - i_1 R = U - i_3 R - i_1 R$$

equal

$$i_2 = i_3 \text{ so } i_1 = 2 \cdot i_2$$

$$U = 12 \text{ V}$$

$$R = 1000 \Omega$$

$$i_2 = \frac{U}{3R} = 4 \text{ mA}$$

$$i_2 + i_3 = 4 \text{ mA}$$

$$\text{therefore } i_1 = 8 \text{ mA}$$

Total Power Consumed  
in Resistors

$$i_2^2 R + i_3^2 R + i_1^2 R$$

$$= (16 + 16 + 64) 1000 \times 10^{-6} \text{ W}$$

$$= 96 \text{ mW}$$

#3.2

a)

$$I_1 r_1 - I_2 r_2 + E_2 - E_1 = 0$$

$$0.25 I_1 - 0.25 I_2 + 1.5 - 1.5 = 0$$

Loop 1 Abcfa

$$I_1 = I_2$$

Loop 2 fcdet  $I_2 r_2 + (I_1 + I_2) R - E_2 = 0$

Substitute  $I_2$  because  $I_1 = I_2$  so

$$I_2 r_2 + (I_2 + I_2) R - E_2 = 0$$

$$0.25 I_2 + (I_2 + I_2)(50) - 1.5 = 0$$

$$I_2 = 0.015 \text{ A}$$

$$I = \text{Current} = I_1 + I_2 \text{ which is } I_2 + I_2 = 2(0.015 \text{ A}) = \boxed{0.030 \text{ A}}$$

b.)

$$I = 2q/t \quad q = 2.5 \text{ A hr}$$

$$t = 2q/I = \frac{2(2.5)}{0.030} = \boxed{166.67 \text{ hrs.}}$$

#4.1

a. Into the page and to the left.

By applying the <sup>left</sup> hand rule we find that this particle therefore must be moving upward which is the positive direction and therefore the particle is positive.

b. It's strange it was an electron because it was found to be a positively charged particle so therefore it must be an antiparticle or an electron.

$$c. F = qvB \sin \theta \quad F = 1.6 \times 10^{-19} \times 10^6 \times \sin(90) =$$

$F = 6.0 \times 10^{-15} \text{ N}$   
Direction of Force is to the left based on our findings in part a.