

# Algebra-Based Physics: Electricity, Magnetism, and Modern Physics (PHYS135B): Unit 1

---

Jordan Hanson

November 7, 2023

Whittier College Department of Physics and Astronomy

## Summary

---

# Unit 1 Summary

Reading: Chapters 19.4 - 19.7, 20.1 - 20.5, 20.7

## 1. Capacitors and capacitance

- Equipotential lines
- Capacitance
- Capacitors

## 2. Current and DC circuits


- DC current, resistance, Ohm's law
- Energy and power in DC current
- AC current and waveforms

# Equipotential Lines and Capacitance

---

# Equipotential Lines

**Equipotential lines** represent locations of constant potential, and run perpendicular to electric field lines.

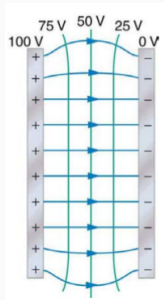

**Figure 1:** Equipotential lines in a parallel plate capacitor.

PhET *demonstration*:

<https://phet.colorado.edu/en/simulations/charges-and-fields>

# Capacitance

What voltage is required to store  $Q$ ? Let  $\Delta V$  be the voltage difference,  $E$  be the electric field strength, and  $\Delta x$  be the capacitor voltage. We already know that

$$\Delta V = E \Delta x \quad (1)$$

We observe that the voltage is linear, so the E-field is constant and proportional to charge per unit area<sup>1</sup>

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A} \quad (2)$$

Substitute  $E$  for  $Q/(\epsilon_0 A)$ , and solve for  $Q$ :

$$Q = \left( \frac{\epsilon_0 A}{\Delta x} \right) \Delta V \quad (3)$$

The term in parentheses is called *the capacitance*,  $C$ .

---

<sup>1</sup>Professor: we can prove this if time permits.

# Capacitance

Let the capacitor have an area  $A$ , and plate separation  $d$ . The capacitance is

$$C = \frac{\epsilon_0 A}{d} \quad (4)$$

$$Q = C\Delta V \quad (5)$$

*Capacitance* represents the ability to store charge. The unit of capacitance is **the farad**, after Michael Faraday (encounter mid-semester). Scaling problems in a moment...

## PhET Activity: Capacitor Basics

---



Go to the activity:

<https://phet.colorado.edu/en/simulation/capacitor-lab-basics>

1. Go to the capacitance tab to find a capacitor and battery.
2. Charge the capacitor under different conditions:  $d = 10$  mm,  $d = 2$  mm,  $A = 100$  mm<sup>2</sup>,  $A = 400$  mm<sup>2</sup>.
3. The **voltmeter** at right is the yellow and black tool. It allows the measurement of voltage between two points. Measure the battery voltage and the capacitor voltage. Why are they equal?
4. What is the charge stored for  $d = 2$  mm, and  $A = 400$  mm<sup>2</sup>?
5. The light bulb tab in the bottom center contains a circuit that operates a light bulb with the energy stored in the capacitor. Measure the voltage across the lightbulb as it is powered with the capacitor. Sketch the voltage as a function of time.

# Capacitance

Two capacitors store the same charge. One only needs half the voltage, though. What is true of the capacitor with the lower voltage?

- A: It has half the capacitance
- B: It has the same capacitance but more charges
- C: It has twice the capacitance
- D: It has half the energy

# Capacitance

Two capacitors have the same capacitance. Capacitor 1 has half the area  $A$  as capacitor 2. Which of the following is true of capacitor 2?

- A: The plates are half the distance ( $\Delta x$ ) apart
- B: The plates are twice the distance ( $\Delta x$ ) apart
- C: The plates have half the voltage
- D: The plates have twice the voltage

# Capacitance

Two identical capacitors power two light bulbs. Capacitor 1 powers the bulb for 20 seconds, and capacitor 2 powers the bulb for 10 seconds. Which of the following is true?

- A: Capacitor 1 was charged at a lower voltage than capacitor 2
- B: Capacitor 1 was charged at the same voltage as capacitor 2
- C: Capacitor 1 was charged at a higher voltage than capacitor 2
- D: Capacitor 2 was not charged

## PhET Activity: Capacitor Lab

---

## PhET Activity: Capacitor Lab

Similar to *Capacitor basics* activity:

<https://phet.colorado.edu/en/simulations/circuit-construction-kit-ac>

What is the relationship between total capacitance and individual capacitances?

1. How do capacitors add *in series*?
2. How do capacitors add *in parallel*?

# PhET Activity: Capacitor Lab

## Instructions:

1. Click the Lab tab. Click and drag three capacitors from the white column at left into the main area.
2. Click on each capacitor and minimize the capacitance to 0.05 F.
3. Orient each capacitor *vertically*, and connect the top sides of the capacitors with wires.
4. Connect the bottom sides of the capacitors with wires.
5. Click and drag a battery from the white column at left into the main area, and do the same for a switch.
6. Connect the battery to the first capacitor, and add a switch between the battery and first capacitor.
7. Leave the switch open.

# PhET Activity: Capacitor Lab

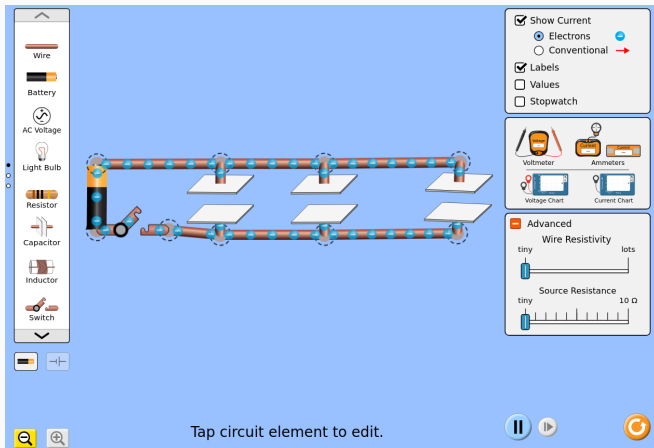


Figure 2: Three capacitors connected in parallel.



# PhET Activity: Capacitor Lab

## Instructions:

1. Click and drag a light bulb from the white column at left, and use wires to connect it to the final capacitor via a switch.
2. Leave both switches open. If your capacitors are charged, close the light bulb switch until the capacitors are fully discharged.
3. With both switches open, close the battery switch to charge the capacitor.
4. Click and drag the voltage charge tool from the white column at right, and place the red and black probes on either side of the light bulb.

# PhET Activity: Capacitor Lab

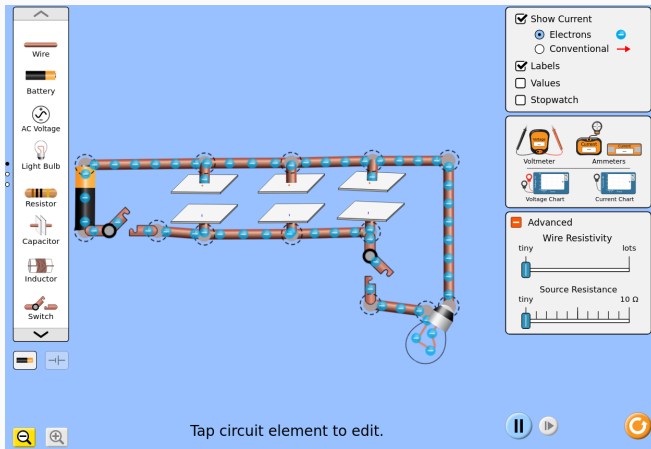


Figure 3: Three capacitors in parallel, with light and switch.

# PhET Activity: Capacitor Lab

## Instructions:

1. Click stopwatch in the white column on the right side.
2. Use the **voltage chart** tool to measure *how long* it takes for the bulb to drain the three capacitors, according to the chart and stopwatch.
  - 2.1 Since your capacitors are charged, leave the battery switch open and close the light bulb switch. Just after closing the switch, click the play button on the stopwatch.
  - 2.2 Measure the average time required for the bulb voltage to drop to zero by collecting 10 measurements.

# PhET Activity: Capacitor Lab

## Instructions:

1. Now we will repeat the same experiment, but with the capacitors connected *in series*.
2. Rearrange the circuit so that the bottom of the first capacitor connects to the top of the second, and the bottom of the second connects to the top of the third. Connect the bulb to the bottom capacitor, and add a switch to the other side of the bulb.
3. Connect the top of the top capacitor to the switch, but leave the switch open.
4. Using separate wires, connect the battery to the top and bottom of the circuit, and add a switch to one side of the battery. Leave both switches open.

# PhET Activity: Capacitor Lab

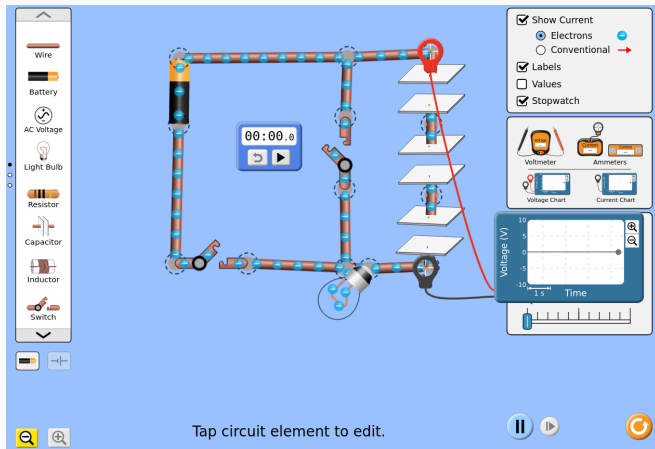


Figure 4: Three capacitors in series, with light and switch.

## PhET Activity: Capacitor Lab

1. Use the **voltage chart** tool to measure *how long* it takes for the bulb to drain the three capacitors, according to the chart and stopwatch.
  - 1.1 Charge the capacitors by closing the battery switch, and then leave it open.
  - 1.2 Close the light bulb switch. Measure the average time required for the bulb voltage to drop to zero by collecting 10 measurements.
2. Which capacitor arrangement takes longer to drain?
3. Given that we used the same voltage for both arrangements, which arrangement (parallel or series) stores more charge?

# Energy in Capacitors

---

# Energy in Capacitors

Energy stored in a *an electric field*,  $\mathcal{E}$ :

$$\mathcal{E} = \frac{1}{2}\epsilon_0 E^2 \quad (6)$$

The proof of Eq. 6 will come later in the course. We also know that the E-field is constant because the voltage is linear. In a parallel-plate capacitor,  $E = \sigma/\epsilon_0 = Q/(\epsilon_0 A)$ . Use  $Q = CV$  and Eq. 6 to show that the total energy in a capacitor with capacitance  $C$  is

$$U_C = \frac{1}{2} \frac{Q^2}{C} \quad (7)$$

$$U_C = \frac{1}{2} CV^2 \quad (8)$$

**Observe proof on board.** The variable  $\sigma$  is known as the *surface charge density*.



# Energy in Capacitors


Suppose we have a 10 nF capacitor at 5V. How many Joules are stored in it?

- A: 100 nJ
- B: 100 pJ
- C: 125 nJ
- D: 125 pJ

# Capacitors, Series and Parallel

---

# Capacitors, Series and Parallel

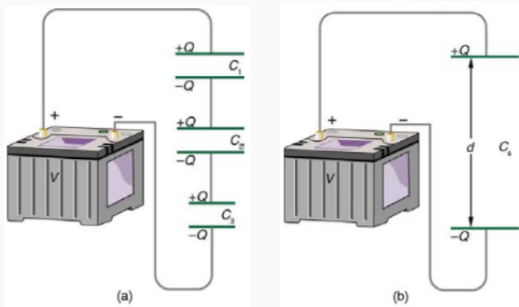

**Figure 5:** How do we compute the total capacitance of (a) such that we know the charge stored for a given voltage in (b)?

# Capacitors, Series and Parallel

Notice that *charge is conserved*, so  $Q$  has to be the same on all capacitors But that means the *voltage* on the different capacitors has to obey

$$Q = Q_1 = Q_2 = Q_3 \quad (9)$$

$$C_{\text{tot}} V_{\text{tot}} = C_1 V_1 = C_2 V_2 = C_3 V_3 \quad (10)$$

To conserve energy, we know that



$$V_{\text{tot}} = V_1 + V_2 + V_3 \quad (11)$$

$$\frac{Q}{C_{\text{tot}}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \quad (12)$$

$$\boxed{\frac{1}{C_{\text{tot}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} \quad (13)$$

This is the how that capacitance adds for capacitors **in series**.

# Capacitors, Series and Parallel

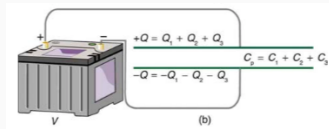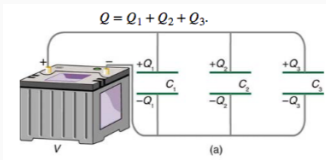

**Figure 6:** How do we compute the total capacitance of (a) such that we know the charge stored for a given voltage in (b)?

## Capacitors, Series and Parallel

Note that all the capacitors are at the same voltage, because wires are equipotentials. Thus,

$$V_{\text{tot}} = V_1 = V_2 = V_3 = V \quad (14)$$

The total charge stored is

$$Q_{\text{tot}} = Q_1 + Q_2 + Q_3 \quad (15)$$

$$C_{\text{tot}}V = C_1V + C_1V + C_2V \quad (16)$$

$$\boxed{C_{\text{total}} = C_1 + C_2 + C_3} \quad (17)$$

This is the how that capacitance adds for capacitors **in parallel**.

## Current

---

# Current

## Notions of current:

- $I = \frac{\Delta Q}{\Delta t}$  - The derivative of charge
- The *movement* of electrons
- The *flow* of charge
- Number of Coulombs per second (1 Amp = C/s)

## One problem:

- Speed of typical electronic signals:  $\approx 10^8$  m/s
- Typical speed of actual charges passing through a conductor under voltage:  $\approx 10^{-4}$  m/s

Since there is a 12 order of magnitude range, it's probably a good idea to ponder...Observe proof on board.



# Ohm's Law

---

# Ohm's Law

Energy is transferred to objects that are not perfect conductors in a *simply connected circuit*:

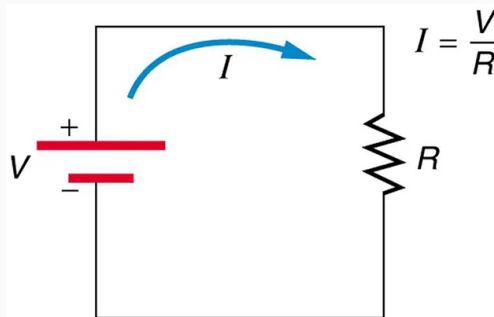


Figure 7: Current transfers energy to *resistors*.

# Ohm's Law

## Ohm's Law

In a simply connected circuit with *resistance*  $R$ , voltage  $V$  and current  $I$ :

$$V = IR \quad (18)$$

**Instructor:** Perform these examples:

- Solve for resistance, observing current.
- Solve for current, observing resistance.
- (We usually take the voltage as a given).

*Time permitting:* How is the energy transferred?

[https://youtu.be/bHIhgXav9LY?si=k1KSrgal\\_x0Nb0mn](https://youtu.be/bHIhgXav9LY?si=k1KSrgal_x0Nb0mn)

# Energy in Capacitors

Suppose we are powering a simple circuit with a DC power supply that allows us to tune the voltage. If we have a resistance  $R$  and a current  $I$ , what will the new current be if we double the voltage?

- A:  $0.5I$
- B:  $1.0I$
- C:  $2.0I$
- D:  $4.0I$

# Energy in Capacitors

Suppose we are powering a simple circuit with a battery. If we have a resistance  $R$  and a current  $I$ , what will the new current be if we double the resistance?

- A:  $0.5I$
- B:  $1.0I$
- C:  $2.0I$
- D:  $4.0I$

## PhET Activity: DC Circuits and Ohm's Law

---

## PhET Activity: DC Circuits and Ohm's Law

Go to the activity: <https://phet.colorado.edu/en/simulation/circuit-construction-kit-dc>

1. Place a battery and connect to it a wire, and attach a resistor to that wire. The resistors are the brown objects with colorful stripes.
2. To the other end of the resistor, connect a switch and leave it open.
3. Connect a light bulb to the other end of the switch, and connect a wire from the light bulb to the battery.
4. The properties of each circuit element can be edited by clicking on the element.

# PhET Activity: DC Circuits and Ohm's Law

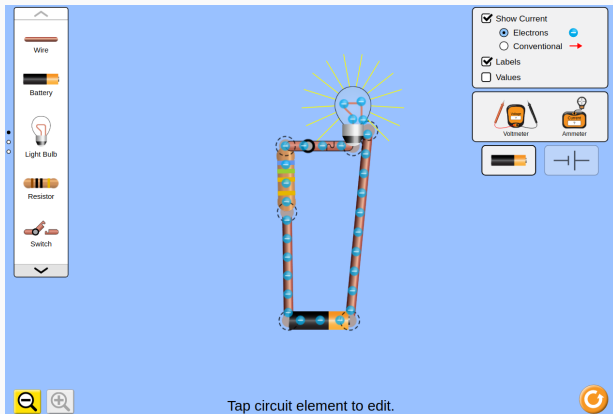


Figure 8: An example of our simply connected circuit.



## PhET Activity: DC Circuits and Ohm's Law

1. What happens to the drift velocity of the electrons as you raise and lower the resistance? Why do we call light bulbs and the brown striped objects “resistors?” Make a sketch of what you think the speed vs. resistance is.
2. How does the current change if you increase the voltage? Make a sketch of what you think the speed vs. voltage is.
3. The voltmeter is a tool to measure the potential difference between two points. Measure voltages around the circuit by touching the black lead to the negative side of the battery, and the red lead to a point in the circuit. This measures  $\Delta V = V_{\text{point}} - V_{\text{minus}} = V_{\text{point}} - 0$ , since we traditionally label the negative side of the battery at 0V.
4. Draw the circuit, and label each section of the circuit with the measured voltage.

## PhET Activity: DC Circuits and Ohm's Law

The unit of resistance is the Ohm. We use the symbol  $\Omega$  for Ohms, and  $1\Omega = 1\text{V/A}$ .

1. An *ammeter* is a device used to measure current. Using the ammeter, measure the current flowing through the circuit at various points.
2. For fixed resistance, take 15 measurements of current as you vary the voltage. The voltage can be varied by clicking on the battery and adjusting the slider. Plot voltage vs. current in Excel, and calculate the slope.
3. What is the number for the slope? How does it compare to the resistor value?

## PhET Activity: DC Circuits and Ohm's Law

**How do we deal with complex circuits?** There must be a way to “add” resistors like we added capacitors.

1. Create a circuit that involves two resistors *in series*.
2. Calculate the *effective total resistance* by plotting an  $i - V$  curve of the system. Measure  $i$  and  $V$  by changing the voltage and using the voltmeter and ammeter. What is a rule for obtaining the total resistance for a group of resistors in series?
3. Create a circuit that involves two resistors *in parallel*.
4. Calculate the *effective total resistance* by plotting an  $i - V$  curve of the system. Measure  $i$  and  $V$  by changing the voltage and using the voltmeter and ammeter. What is a rule for obtaining the total resistance for a group of resistors in parallel?

For these exercises, it's helpful to use resistors of the same value.


## DC Circuits and Ohm's Law

As you may have discovered, *resistors in series* **add**:

$$R_{\text{tot}} = R_1 + R_2 + \dots \quad (19)$$

*Resistors in parallel* **add their reciprocals**:

$$\frac{1}{R_{\text{tot}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \quad (20)$$

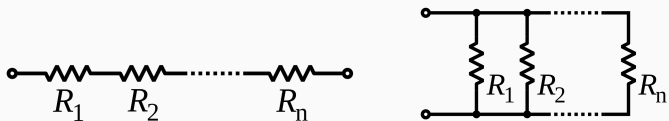

**Figure 9:** (Left) These are resistors in series. (Right) These are resistors in parallel.

## DC Circuits and Ohm's Law

Resistance is not an *intrinsic property* of materials. Imagine a 0.1 m-long wire (which is a conductor) actually having a small resistance. What about that same wire, but 1 kilometer long?


### Observations:

- Resistance depends on the length of a given material
- Resistance depends on the thickness of a given material

**Resistivity**  $\rho$  is defined in terms of resistance  $R$ , length  $L$  and cross-sectional area  $A$  as

$$R = \rho \left( \frac{L}{A} \right) \quad (21)$$

# DC Circuits and Ohm's Law

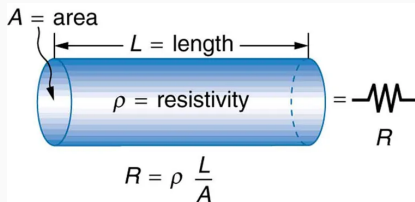

**Figure 10:** Resistivity has units of  $\Omega \text{ m}$ , and resistance depends on resistivity, area, and length.

Material	Resistivity [ $\Omega \text{ m}$ ]
Silver	$1.59 \times 10^{-8}$
Copper	$1.72 \times 10^{-8}$
Silicon (pure)	2300
Silicon (doped)	0.1 – 2300
Wood	$10^8 - 10^{11}$

**Table 1:** Resistivity for conductors, semi-conductors, and insulators.

A copper wire carrying current to the top floor of a building, that has a cross-sectional area of  $12 \text{ mm}^2$  and is 100 meters long. The resistivity of copper is  $1.7 \times 10^{-8} \Omega \text{ m}$ . What is the resistance of the wire?

- A: about  $1 \text{ m}\Omega$
- B: about  $10 \text{ m}\Omega$
- C: about  $100 \text{ m}\Omega$
- D: about  $1 \Omega$

Consider the same system. If we attach a battery and use the wire to feed voltage to some circuit drawing 3.0 A of current, what is the voltage drop ( $-IR$ ) due to just the wire?

- A: about 0.003V
- B: about 0.03V
- C: about 0.3V
- D: about 0V

*So you can start to see that resistance matters even for conductors, if the current is traveling for long distances. Often manufacturers quote the Ohms per foot in wire data sheets.*



# Energy and Power in DC Current

---

## Energy and Power in DC Current

Recall that **power** is consumed in resistors, since charges are losing energy and new charges are showing up at a certain rate. Consider the PE converted to work in a resistor:

$$\Delta PE = \Delta q \Delta V \quad (22)$$

$$\Delta W = \Delta q I R \quad (23)$$

$$\frac{\Delta W}{\Delta t} = \frac{\Delta q}{\Delta t} I R = I^2 R \quad (24)$$

$$\frac{\Delta W}{\Delta t} = I V \quad (25)$$

$$P = I V \quad (26)$$

The formula  $P = IV$  relates the current drawn at a given voltage by a device, resistance, or “load” that requires a given power to operate.

## Energy and Power in DC Current

How much current is required by a 50 W light bulb if the voltage supplying it is 120 V?

- A: 420 mA
- B: 120 mA
- C: 50 mA
- D: 50 V

# Energy and Power in DC Current

A *fuse* is a device that disconnects a circuit if the current rises above a pre-defined value. Some fuses have a wire that is rated to melt at a given current such that the circuit is no longer closed. Suppose a device rated to consume 50 W is connected to a 12 V battery, in series with a fuse that is rated to blow at 1 A. Does it blow?

- A: Yes
- B: No

## Energy and Power in DC Current

Suppose two devices rated at 50 W are connected to a 12 V battery *in parallel*. Between these devices and the battery is a fuse that is rated to blow at 10 A. Does it blow?

- A: Yes
- B: No

## Energy and Power in DC Current

Note that energy is power multiplied by time:

$$P = \frac{\Delta W}{\Delta t} \quad (27)$$

$$P\Delta t = \Delta W \quad (28)$$

$$P[kW] \Delta t[hr] = \Delta W \quad (29)$$

In the last line, we are simply committing to using kiloWatts and hours as our units.

Suppose the cost per unit energy in electricity in our area is stated as \$0.15/(kW hr). Remember that the kiloWatt-hour is a unit of *energy*.

## Energy and Power in DC Current

(a) What is the total cost (capital plus operation) of using a 50-W incandescent bulb for 2000 hours (the lifetime of that bulb) if the bulb cost \$0.40? (b) If we choose a compact fluorescent light that provides the same light output, but at 10W, and which costs \$1.20 but lasts 10,000 hours, what will that total cost be?

What is an equitable way to compare these two products?


**Solve this together in groups.**

# AC Circuits and Waveforms

---




# AC Circuits and Waveforms

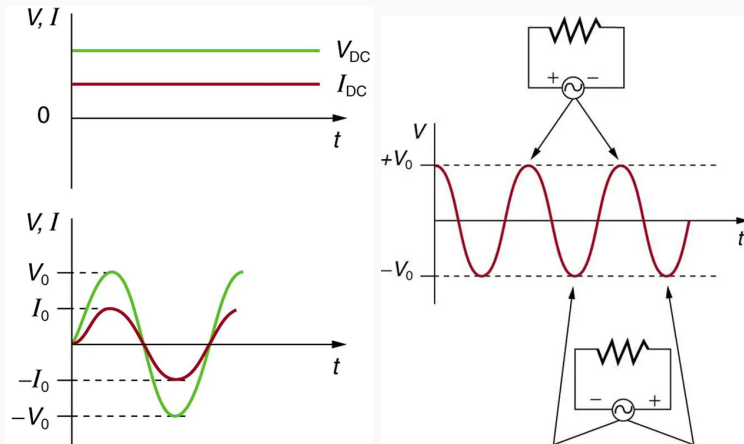

**Figure 11:** Alternating current (AC) circuits involve voltages and currents that change polarity and depend on time. (Left) DC and AC current, voltage, vs. time. (Right) Polarity changes over time.

# AC Circuits and Waveforms

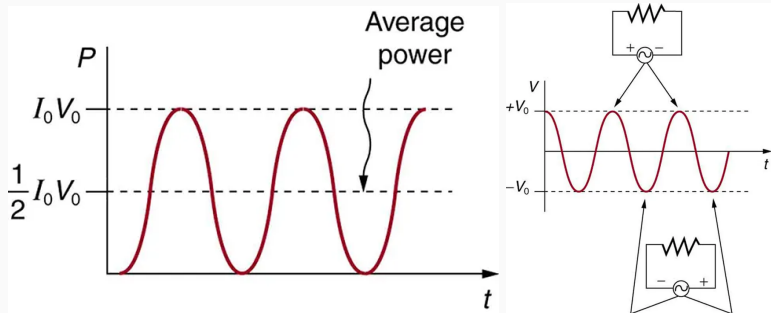

**Figure 12:** Power in an AC circuit is greater than or equal to zero, and also depends on time. (Right) Polarity changes over time.

**Power is consumed** regardless of polarity by a load resistance.

# AC Circuits and Waveforms

## Components of an oscillating signal

In a simply connected AC circuit:

$$V(t) = V_0 \sin(2\pi ft) \quad (30)$$

- $V_0$  is the *amplitude* in volts.
- $f$  is the *frequency* in Hertz ( $\text{sec}^{-1}$ ).
- $t$  is the *time* in seconds.
- $V_0$  is zero when  $2\pi ft = n\pi$ , or when  $t = \frac{1}{2f} = \frac{T}{2}$ .
- $T = 1/f$  is the *period* of the wave.

# AC Circuits and Waveforms

AC signals at a single frequency  $f$

In a simply connected AC circuit:

$$V(t) = V_0 \sin(2\pi ft) \quad (31)$$

$$I(t) = I_0 \sin(2\pi ft) \quad (32)$$

$$P(t) = V(t)I(t) = V_0 I_0 \sin^2(2\pi ft) \quad (33)$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}, \quad I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \quad (34)$$

$$P_{\text{ave}} = \frac{1}{2} V_0 I_0 \quad (35)$$

If we generate an alternating voltage at  $V_0 = 120 \text{ V}$  and  $f = 60 \text{ Hz}$ , what is the *period*?

- A: 6 seconds
- B:  $1/6$  seconds
- C: 60 seconds
- D:  $1/60$  seconds

If we generate an alternating voltage at  $V_0 = 120 \text{ V}$  in a simple circuit, and  $R = 6 \text{ k}\Omega$ , what is the *maximum* current?

- A: 0.02 Amps
- B: 0.2 Amps
- C:  $0.02/\sqrt{2}$  Amps
- D:  $0.2/\sqrt{2}$  Amps

If we generate an alternating voltage at  $V_0 = 120 \text{ V}$  in a simple circuit, and  $R = 6 \text{ k}\Omega$ , what is the *rms* current?

- A: 0.02 Amps
- B: 0.2 Amps
- C:  $0.02/\sqrt{2}$  Amps
- D:  $0.2/\sqrt{2}$  Amps

## PhET Activity: AC Circuits and Waveforms

PhET activity on AC circuits and waveforms:

<https://phet.colorado.edu/en/simulations/circuit-construction-kit-ac>

What is the relationship between voltage and current in AC circuits?

1. Click the AC Voltage tab.
2. Create a simple circuit with a resistor, wires, and an AC voltage source.
3. Include a switch so you can turn the circuit off and on.
4. The AC voltage source is the white component with plus/minus signs and the wave symbol.



# PhET Activity: AC Circuits and Waveforms

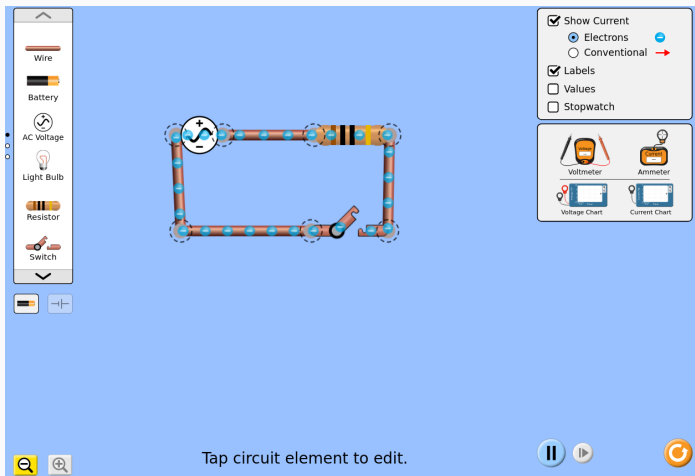


Figure 13: Your circuit should resemble this one.

## PhET Activity: AC Circuits and Waveforms

What is the relationship between voltage and current in AC circuits?

1. Use the voltage chart to plot voltage versus time.
2. Use the current chart to plot current versus time.

Measure the following:

- The period of the current.
- The period of the voltage.
- The maximum voltage.
- The maximum current.
- What is the ratio of max voltage to max current? How does this compare to resistance?

# PhET Activity: AC Circuits and Waveforms

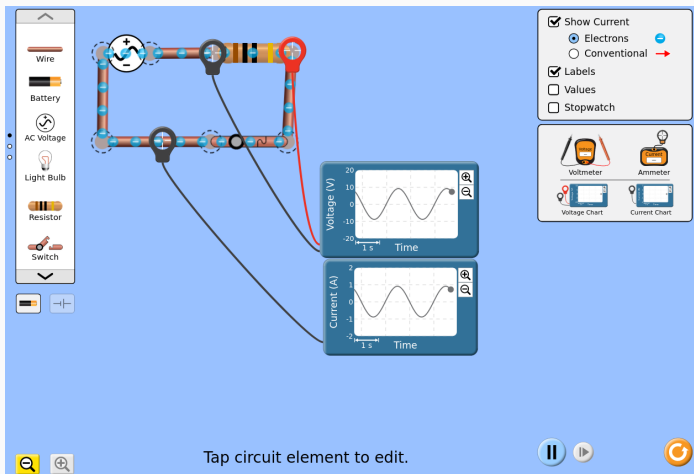


Figure 14: Your circuit should resemble this one.

## Conclusion

---

# Unit 1 Summary

Reading: Chapters 19.4 - 19.7, 20.1 - 20.5, 20.7

## 1. Capacitors and capacitance

- Equipotential lines
- Capacitance
- Capacitors

## 2. Current and DC circuits

- DC current, resistance, Ohm's law
- Energy and power in DC current
- AC current and waveforms