

2 Chapter 9: Current and Resistance

1. An ECG monitor must have an RC time constant less than $100\mu\text{s}$ to be able to measure variations in voltage over small time intervals. (a) If the resistance of the circuit (due mostly to that of the patient's chest) is $1.00\text{ k}\Omega$, what is the maximum capacitance of the circuit? (b) Would it be difficult in practice to limit the capacitance to less than the value found in (a)? (c) If the patient's resistance really is $1.00\text{ k}\Omega$, and the typical maximum amplitude of the patient's heartbeat is 60 mV , when does the voltage rise to 30 mV in the EKG monitor (using the C you found in (a))?

$$C = \frac{100 \times 10^{-6} - 0}{100 \times 10^3} = 100 \times 10^{-9} \text{ F} = 100 \text{ nF}$$

$$100 \times 10^{-9} = 100 \text{ nF}$$

$$100 \times 10^{-9} = 100 \text{ nF}$$

$$100 \times 10^{-9} = 100 \text{ nF}$$

2. Imagine an alternating current (AC) system, as opposed to the DC systems we normally consider. In AC circuits, the voltage follows a form

$$V(t) = V_0 \sin(2\pi ft + \phi)$$

The wall outlets in the USA have $f = 60\text{ Hz}$ and $V_0 = 120\text{ V}$. We have the freedom to choose ϕ in this example, much like choosing the zero-point of voltage. (a) Suppose $\phi = 0$. At what times will $V(t) = 0$? (b) What is the max power delivered to a $1\text{ k}\Omega$ resistor? (c) What is the average power delivered to a $1\text{ k}\Omega$ resistor?

$$V(t) = 120 \sin(2\pi \cdot 60 t)$$

$$V(t) = 120 \sin(120\pi t)$$

$$V(t) = 120 \sin(120\pi t)$$

$$V(t) = 120 \sin(120\pi t)$$

3. For those of us stuck at home! A physics student has a single-occupancy dorm room. The student has a small refrigerator that runs with a current of 3.00 A and a voltage of 110 V , a lamp that contains a 100-W bulb, an overhead light with a 60-W bulb, and various other small devices adding up to 3.00 W . In Southern California, electricity costs about 0.2 dollars per kilowatt-hour. How much money does this student spend if the total wattage is on for 12 hours per day for one month?

$$(177.5 \text{ kWh}) (0.2) = 35.5 \text{ dollars}$$

$$177.5 \text{ kWh} = 177.5 \times 1000 \text{ Wh} = 177,500 \text{ Wh}$$

$$177,500 \text{ Wh} = 177.5 \text{ kWh}$$

3 Chapter 10: Direct-Current (DC) Circuits

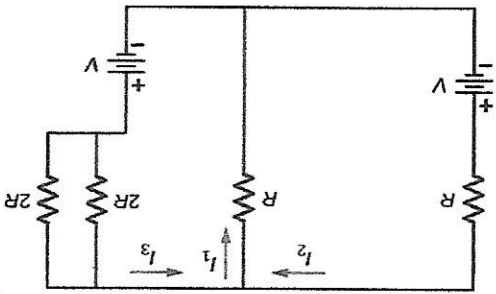


Figure 1: A circuit with two batteries and three resistors.

1. Solve for i_1 , i_2 , and i_3 in Fig. 1, if $R = 1\text{ k}\Omega$, and $V = 12.0\text{ Volts}$. What power is consumed in the resistors?

$$I_1 = 96 \text{ mA}$$

$$I_2 = 96 \text{ mA}$$

$$I_3 = 96 \text{ mA}$$