

$$T = RC \quad C = \frac{T}{R}$$
$$C = \frac{100 \times 10^{-6} \text{ s}}{1.00 \times 10^3 \Omega} = (1.0 \times 10^{-7} \text{ F}) \left( \frac{1.0 \times 10^9 \text{ nF}}{1 \text{ F}} \right)$$
$$= 1.0 \times 10^{-7} \text{ F or } 100 \text{ nF}$$

The maximum capacitance is  $1.0 \times 10^{-7} \text{ F}$  or  $100 \text{ nF}$ .

- b) It would not be difficult to limit the capacitance, because you can easily limit the capacitance of the capacitor range from  $\text{nF}$  to  $\text{mF}$  in the ECG monitor system. One way of doing this is by adding more resistance.

c)  $R = 1000 \Omega$ , max amp =  $60 \text{ mV}$   $C = 1.0 \times 10^{-7} \text{ F}$

$$RC = (1000 \Omega)(1.0 \times 10^{-7} \text{ F}) = 1.0 \times 10^{-4}$$

\* remember  $t = RC$  \*

$$V_C(t) = \mathcal{E}_0 (1 - e^{-t/\tau}) \quad \tau = 1.0 \times 10^{-4}$$

$$\frac{0.003 \text{ V}}{0.006 \text{ V}} = \frac{0.006 \text{ V} (1 - e^{-t/1.0 \times 10^{-4} \text{ s}})}{0.006 \text{ V}}$$

$$0.5 \text{ V} = 1 - e^{-t/1.0 \times 10^{-4} \text{ s}}$$

$$\ln(e^{-t/1.0 \times 10^{-4} \text{ s}}) = \ln(0.5)$$

$$1.0 \times 10^{-4} \times \frac{-t}{1.0 \times 10^{-4} \text{ s}} = \ln(0.5)$$

$$-t = \ln(0.5)(1.0 \times 10^{-4} \text{ s})$$

$$-t = -6.93 \times 10^{-5}$$

$$t = 6.93 \times 10^{-5} \text{ sec}$$

$$V(t) = V_0 \sin(2\pi f t + \phi) \quad V_0 = 120 \text{ V}$$

a)  $V(t) = 120 \sin(2\pi f t) \therefore f = 60 \text{ Hz}$   
 $\phi = 0$   
 $V(t) = 0$  and when

$$\sin(2\pi f t) = \sin(2\pi n)$$

where  $n$  is any real number  
 such as 0, 1, 2...  $\boxed{t = \frac{n}{f}}$

b)  $R = 1000 \Omega$   $\frac{V}{R} = \frac{IR}{R}$   $\frac{\Delta V}{R} = \Delta I = V(t)$

$$i(t) = \frac{V(t)}{R} \sin(2\pi f t + \phi)$$

$$i(t) = \frac{120 \text{ V}}{1000 \Omega} (\sin(2\pi(60)(t) + \phi))$$

$$i(t) = 0.12 \text{ A} \quad \text{now remembering } P = IV \text{ and } V = IR$$

$$\therefore P = I^2 R$$

$$P = (0.12 \text{ A})^2 \times 1000 \Omega$$

$$\boxed{P = 14.4 \text{ Watts}}$$

c)  $P = \frac{(0.12 \text{ A})^2 \cdot 1000 \Omega}{2}$   $V = \frac{IR}{2}$

$$P = \frac{(I)^2 R}{2} \quad \text{where } I^2 = 0.0144 \text{ A} \text{ and } R = 1000 \Omega$$

$$P = \frac{0.0144 \text{ A} \times 1000 \Omega}{2}$$

$$\boxed{P = 7.2 \text{ Watts}}$$

2



3.  $I = 3.00 \text{ A}$  and  $P = IV$   
 $V = 110 \text{ V}$

$$P = (3.00 \text{ A})(110 \text{ V})$$

$$= 330 \text{ Watts}$$

$$P_{\text{total}} = 330 \text{ W} + 60 \text{ W} + 100 \text{ W} + 3.00 \text{ W}$$

$$= 493 \text{ W}$$

$$= 0.493 \text{ kW}$$

$$0.493 \text{ kW} \times \frac{\$0.2}{\text{kW} \cdot \text{hr}} \times \frac{12 \text{ hr}}{1 \text{ day}} \times 30 \text{ days}$$

The student spends  
 $\approx \$35.50$

On 10 (1)  $R = kR$ ,  $V = 12 \text{ V}$  and  $I = \frac{V}{R}$

$$I_1 = (I_2 + I_3)$$

$$E - I_3 \left( \frac{1}{2R} + \frac{1}{2R} \right) - I_1 R = 0$$

$$= E - I_3 \left( \frac{1}{2R} + \frac{1}{2R} \right) - (I_2 + I_3) R = 0$$

$$E - I_3 \left( \frac{1}{2R} + \frac{1}{2R} \right) + I_2 R + I_3 R = 0$$

$$E - I_3 \left( \frac{1}{2R} + \frac{1}{2R} + R \right) + I_2 R = 0$$

$$12 \text{ V} = I_3 (1000 \Omega + 1000 \Omega)$$

$$\frac{1}{R} = \frac{1}{2R} + \frac{1}{2R}$$

$$R = \frac{2R}{2} = 1000 \Omega$$

$$12 \text{ V} = I_3 (2000 \Omega) + 1000 R I_2$$

now remembering that  $I_1 = I_2 + I_3$

we can plug into  $E - I_2 R - I_1 R = 0$

$$E - I_2 R - (I_2 + I_3) R = 0$$

$$E - I_2 R - I_2 R - I_3 R = 0$$

(3)

$$E = I_2 R + I_2 R + I_3 R \quad A \cdot 0.8 = I$$

$$E = I_2 (R + R) + I_3 R$$

$$12 \text{ V} = I_2 (2000 \Omega) + 1000 \Omega \times I_3$$

using the eqns in purple

$$2(12 \text{ V}) = (2000 \Omega I_2 + 1000 \Omega I_3) 2$$

$$24 \text{ V} = 4000 \Omega I_2 + 2000 \Omega I_3$$

$$12 \text{ V} = 1000 \Omega I_2 + 2000 \Omega I_3$$

$$12 \text{ V} = 3000 \Omega I_2 + 0$$

$$\frac{12 \text{ V}}{3000 \Omega} = I_2 \therefore I_2 = 0.004 \text{ A} !$$

now that we have  $I_2$  we can solve for  $I_3$  &  $I_1$ .

$$12 \text{ V} = 1000 \Omega I_2 + 2000 \Omega I_3$$

$$12 \text{ V} = 1000 \Omega (0.004 \text{ A}) + 2000 \Omega I_3$$

$$12 \text{ V} = \frac{4}{-4} + \frac{2000 \Omega I_3}{-4}$$

$$\frac{8}{2000 \Omega} = \frac{2000 \Omega I_3}{2000 \Omega} \quad I_3 = 0.004 \text{ A} !$$

now that we have  $I_2$  and  $I_3$  we can find  $I_1$  !

$$I_1 = 0.004 \text{ A} + 0.004 \text{ A}$$

$$I_1 = 0.008 \text{ A} !$$

4



now we can solve P for  $I_1, I_2$ , and  $I_3$ !

$$I_1) P = (0.008 A)^2 (1000 \Omega) = 0.064 \text{ Watts}$$

$$I_2) P = (0.004 A)^2 (1000 \Omega) = 0.016 \text{ Watts}$$

now to solve for  $P_{\text{total}}$  since  $P = I_3 (R_{\text{total}})$

$$I_3) P_{\text{tot}} = (0.004 A)^2 (1000 \Omega) = 0.016 \text{ Watts}$$

now that we have total P now we can solve for the power in each resistor

$$\frac{0.016 \text{ Watts}}{2}$$

both resistors

0.008 watts  
for each  
resistor!

ch 10

$$2) \mathcal{E} = 1.5 V \quad r = 0.25 \Omega \quad R = 50 \Omega$$

$$\mathcal{E}_1 - I_1 r_1 + I_2 r_2 - \mathcal{E}_2 = 0 \text{ now rearranging this}$$

$$I_1 r_1 - I_2 r_2 + \mathcal{E}_2 - \mathcal{E}_1 = 0$$

$$0.25 I_1 - 0.25 I_2 + 1.5 - 1.5 = 0$$

and  $\star I_1 = I_2 \star$  will use  $I_2$  to represent  $I_1$  and  $I_2$ !

$$I_2 r_2 + (I_2 + I_2) R - \mathcal{E}_2 = 0$$

$$\star 0.25 I_2 + (I_2 + I_2)(50) - 1.5 = 0$$

$$I_1 \text{ and } I_2 = 0.015 A$$

Since we are solving for current

$$I_{\text{tot}} = I_1 + I_2 = 0.015 + 0.015 = 0.030 A$$

$$\boxed{\text{Current flow} = 0.030 A}$$

5

2b)  $q = 2.5 \text{ A hr}$  since there is 2 batteries  $\hookrightarrow 2q$   
 $\Delta Q = I \Delta t$  and  $I = \frac{2q}{t}$

$$t = \frac{2q}{I} = \frac{2(2.5)}{0.030}$$

$$t = 166.7 \text{ h}$$

Ch 11

- ① Since the particle bends to the left after passing through the plate and the magnetic field is into the plate, we can infer that the particle is moving upward. Furthermore if the particle is moving upwards and again bends to the left, the particle is positively charged.

- b) the mass of the particle (given that it has a mass of an electron as stated) is about  $9.1 \times 10^{-31} \text{ kg}$

This information however doesn't coincide with the fact that an electron is negatively charged. Therefore, since the mass is positive and an  $e^-$  is negative ( $q = -1.6 \times 10^{-19} \text{ C}$ ) it doesn't seem likely that this particle can have the mass of an electron.

However what could make this hold true is if the particle is an antiparticle in which  $q = +1.6 \times 10^{-19} \text{ C}$

⑥



$$1c) B = 0.05 T, V = 10^6 \text{ m/s}$$

$$q = +1.6 \times 10^{-19} \text{ C}$$

additionally since the angle between  $B$  and  $V$  is  $90^\circ$

we can now solve this using this equation

$$F = q \times V \times B \sin \theta$$

$$\text{where } \theta = 90^\circ$$

$$\text{and } \sin 90^\circ = 1$$

now

$$F = (1.6 \times 10^{-19} \text{ C}) \times (1.0 \times 10^6 \text{ m/s}) \times (0.05)$$

$$F = 8.0 \times 10^{-15} \text{ N}$$

and the direction of the force is to the left