

Brander Ramos

$$100\text{ns} \times \frac{10^{-6}}{1\text{ns}} = 100 \times 10^{-6}\text{s}$$

#1 $1\text{k}\Omega \times \frac{100\text{aF}}{1\text{k}\Omega} = 100\text{aF}$

a) $RC = T$ $T < 100 \times 10^{-6}\text{s}$

$$(100\text{aF}) C < 100 \times 10^{-6}\text{s}$$

$$C < \frac{100 \times 10^{-6}\text{s}}{100\text{aF}}$$

$C < 1.0 \times 10^{-7}\text{F}$

b) NO, b/c you can add more resistors to lower the capacitance and the time constant is $T < 1.0 \times 10^{-6}\text{s}$ suit can be used.

Capacitor with low current & capacitance

c) $0, V_C(t) = E_0 (1 - e^{-t/RC})$ $RC = (100\text{aF})(1.0 \times 10^{-7}\text{F})$
 $RC = 1.0 \times 10^{-4}$

$$\frac{0.03\text{V}}{0.06\text{V}} = \frac{0.06\text{V}(1 - e^{-t/1.0 \times 10^{-4}\text{s}})}{0.06\text{V}}$$

$$0.5\text{V} = 1 - e^{-t/1.0 \times 10^{-4}\text{s}} \quad -t = -6.93 \times 10^{-5}$$

$$\ln(e^{-t/1.0 \times 10^{-4}\text{s}}) \quad \ln(0.5)$$

$$1.0 \times 10^{-4} \times \frac{-t}{1.0 \times 10^{-4}\text{s}} = \ln(0.5)$$

$$-t = \ln(0.5)(1.0 \times 10^{-4}\text{s})$$

$$t = 6.93 \times 10^{-5}\text{s}$$

$$a) V(t) = V_0 \sin(2\pi f t + \phi)$$

$$V_0 = 120V; \quad \phi = 0$$

$$V(t) = 120 \sin(2\pi f t)$$

$$\star \sin(2\pi n) = 0 \quad n = 0, 1, 2, 3, \dots$$

$$\sin(2\pi f t) = \sin(2\pi n)$$

$$t = \frac{n}{f}$$

$$\frac{2\pi f t}{2\pi f} = 2\pi n$$

$$t = \frac{2\pi n}{2\pi f}$$

$$b) 1 \text{ k}\Omega \times \frac{1000 \Omega}{1 \text{ k}\Omega} = \underline{1000 \Omega} \quad V_0 = \underline{120 \text{ V}}$$

$$\frac{V}{R} = \frac{I\omega}{R} \quad \frac{\Delta V}{R} = I \quad f = 60 \text{ Hz}$$

* $i(t) = \frac{V(t)}{R} \sin(2\pi f t + \phi)$

$$i(t) = \frac{120 \text{ V}}{1000 \Omega} \left(\sin(2\pi(60 \text{ Hz})(t) + \phi) \right)$$

$$i(t) = 0.12 \text{ A}$$

$$P = IV \quad V = IR$$

$$i(t) = 0.12 \text{ A}$$

$$P = I^2 R$$

$$P = (0.12 \text{ A})^2 \cdot 1000 \Omega$$

$$P = 14.4 \text{ watts}$$

$$P = \frac{(0.12A)^2}{2} \cdot 1000\Omega$$

$$V = \frac{I R}{2}$$

$$P = I V$$

$$P = \frac{(I)^2 R}{2}$$

$$P = \frac{0.0144A \cdot 1000\Omega}{2}$$

$$P = 7.2 \text{ watts}$$

$$\#3 \quad 3.00A = I \quad *P = IV$$

$$110V = V$$

$$P = (3.00A)(110V)$$

$$P = 330 \text{ watts}$$

$$P_{\text{tot}} = 330 \text{ w} + 100 \text{ w} + 60 \text{ w} + 3 \text{ w}$$

$$P_{\text{tot}} = 493 \text{ w} = \frac{0.493 \text{ kW}}{\frac{0.2 \text{ doll}}{\text{kW} \cdot \text{hr}}} \quad *$$

~~$$\frac{1}{12} \times \frac{12 \text{ hr}}{1 \text{ day}} \times \frac{30 \text{ days}}{1 \text{ month}}$$~~

$$0.493 \text{ kW} \cdot \frac{0.2 \text{ doll}}{\text{kW} \cdot \text{hr}} \cdot \frac{12 \text{ hr}}{1 \text{ day}} \cdot \frac{30 \text{ days}}{1 \text{ month}}$$

~~\$35.49~~ in one month

#1

(CH: 10)

$$I_1 = (I_2 + I_3)$$

$$E - I_3 \left(\frac{1}{2R} + \frac{1}{2R} \right) - I_1 R = 0$$

$$E - I_3 \left(\frac{1}{2R} + \frac{1}{2R} \right) - (I_2 + I_3) R = 0$$

$$E = I_3 \left(\frac{1}{2R} + \frac{1}{2R} \right) + I_2 R + I_3 R = 0$$

$$E = I_3 \left(\frac{1}{2R} + \frac{1}{2R} + R \right) + I_2 R = 0$$

$$*R = 1000\Omega$$

$$*V = 12V$$

$$\frac{1}{R} = \frac{1}{2R} + \frac{1}{2R}$$

$$R = \frac{R}{\frac{1}{2}} = 1000\Omega$$

$$12V = I_3 (1000\Omega + 1000\Omega)$$

$$(12V = I_3 (2000\Omega) + 1000\Omega I_2)$$

$$(I_2 + I_3) = I_1$$

$$E - I_2 R - I_1 R = 0$$

$$E - I_2 R - (I_2 + I_3) R = 0$$

$$E - I_2 R - I_2 R - I_3 R = 0$$

$$E = I_2 R + I_2 R + I_3 R$$

$$E = I_2 (R + R) + I_3 R$$

$$12V = I_2 (1200\Omega) + 1000\Omega I_3$$

Elm

$$12V = (2000\Omega I_2 + 1000\Omega I_3) 2$$

$$12V = 1000\Omega I_2 + 2000\Omega I_3$$

Subtract

$$24V = 4000\Omega I_2 + 2000\Omega I_3$$

~~$$12V = 1000\Omega I_2 + 2000\Omega I_3$$~~

$$12V = 3000\Omega I_2 + 0$$

$$\frac{12V}{3000\Omega} = I_2$$

$$0.004A = I_2$$

we can now find I_3 and I_1

$$12V = 1000\Omega I_2 + 2000\Omega I_3$$

$$12V = 1000\Omega (0.004A) + 2000\Omega I_3$$

$$12V = 4 + 2000\Omega I_3$$

$$12 - 4 = 2000\Omega I_3$$

$$\frac{8V}{2000\Omega} = I_3$$

$$I_1 = I_2 + I_3$$

$$0.004A = I_3$$

$$I_1 = 0.004A + 0.004A$$

$$I_1 = 0.008A$$

$$P = (I_1)^2 R$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$P = (I_2)^2 R$$

$$\frac{1}{R} = \frac{2}{2R}$$

$$P = (I_3)^2 (R + \frac{R}{2})$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$R = R$$

$$R = 1000\Omega$$

$$P = (0.008A)^2 (1000\Omega) = 0.064 \text{ watts}$$

$$P = (0.004A)^2 (1000\Omega) = 0.016 \text{ watts}$$

$$P = (0.0041A)^2 (1000\Omega) = 0.016 \text{ watts}$$

total

$$\frac{0.016}{2} = 0.008 \text{ watts}$$

for each

$2R$

So total was

0.064

0.016

0.008

0.008

0.096 watts

(HP: 10)

#2

$$E = 1,5 \text{ V}$$

$$R = 50 \Omega$$

$$r = 0,25 \Omega$$

$$E = I (r + R)$$

a) $E = I \frac{R}{r+R}$

$$\frac{1,5 \text{ V}}{0,125 \Omega + 50 \Omega} = I$$

$$0,0299 = I$$

$$\frac{1}{R} = \frac{1}{0,125} + \frac{1}{50}$$

$$\frac{1}{r} = \frac{2}{r}$$

$$r = \frac{f}{2}$$

$$r = \frac{0,25 \Omega}{2}$$

$$r = 0,125 \Omega$$

b)

$$Q = 2,5 \text{ A} \cdot \text{hr}$$

~~$$I = \frac{Q}{t}$$~~

two charges!!!

$$2,5 \text{ A} \cdot \text{hr} + 2,5 \text{ A} \cdot \text{hr} = 5,0 \text{ A} \cdot \text{hr} = (0,0299 \text{ A}) \Delta t$$

$$\Delta Q = I \Delta t$$

$$5,0 \text{ A} \cdot \text{hr}$$


$$\frac{5,0 \text{ A} \cdot \text{hr}}{0,0299} = \Delta t$$

$$167,123 \text{ hr} = \Delta t$$

a)


Magnetic field is n-to-the
Puye (Bout).

Particle bends to
the left $+(-) = F$

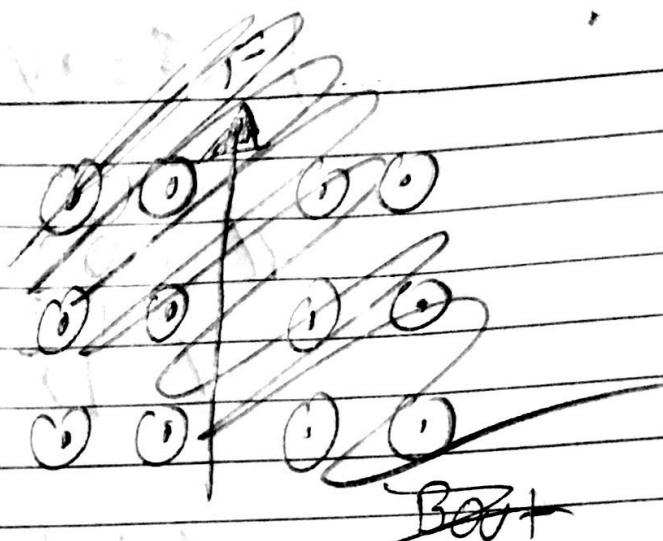

Left hand rule

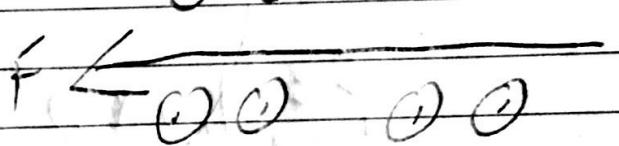Upward motion is
the direction and is
positive (+) charge,



Upwards
positive

* Positively charged
particle

Upwards
positive

$$m = 9.1 \times 10^{-31} \text{ kg}$$

b) Strange ~~material~~ maybe b/c it has
the mass equal to the electron but
however it does not have the same charge.
Electrons are usually charged negative
charged.

* This could possibly be an α particle
or electron so it is $e = (+) 1.6 \times 10^{-19} \text{ C}$

c) ~~$F = qVBS \sin\theta$~~

~~A. $B = 0.05 T$~~

~~$V = 10^6 \text{ m/s}$~~

angle between

Bnd & V is

~~$90^\circ + 11^\circ$~~

$q = +1.6 \times 10^{-19} \text{ C}$

$$F = (1.6 \times 10^{-19} \text{ C})(10^6 \text{ m/s})(0.05 \text{ T}) \sin(90^\circ)$$

$$F = (1.6 \times 10^{-19} \text{ C})(10^6 \text{ m/s})(0.05 \text{ T})(1)$$

~~$F = 8 \times 10^{-18} \text{ N}$~~

* direction is to the left.

Using left hand rule