

Tuesday Reading Assessment: Unit 1, Capacitance

Prof. Jordan C. Hanson

February 25, 2020

1 Memory Bank

- $C = A\epsilon_0/d$... Capacitance of a parallel-plate capacitor.
- $\epsilon_0 = 8.85 \times 10^{-12}$ F/m
- $C_{tot}^{-1} = C_1^{-1} + C_2^{-1}$... Total capacitance of two capacitors in series.
- $C_{tot} = C_1 + C_2$... Total capacitance of two capacitors in parallel.

2 Capacitors

1. Suppose you have a parallel plate capacitor with $A = 1 \text{ mm}^2$, and $d = 0.1 \text{ mm}$. What is the capacitance?
2. Now suppose two identical capacitors from the previous problem are added *in series*. What is the total capacitance?
3. Same question, but they are added *in parallel*. What is the total capacitance?
4. Which of the following should be the formula for the capacitance of a coaxial cable of length L ? The inner and outer radii are R_1 and R_2 , respectively. *Think about the units of ϵ_0 .*
 - A: $C = (2\pi\epsilon_0 R_1 L) / \ln(R_2/R_1)$.
 - B: $C = (2\pi\epsilon_0 L) / \ln(R_2/R_1)$.
 - C: $C = (2\pi\epsilon_0 R_1 R_2 L) / \ln(R_2/R_1)$.
 - D: $C = (2\pi\epsilon_0 L)$.