

# Monday Reading Assessment: Unit 1, Capacitance

Prof. Jordan C. Hanson

February 5, 2024

## 1 Memory Bank

- $Q = CV$  ... Relationship between capacitance, charge, and voltage.
- $C_{tot} = C_1 + C_2 + C_3 + \dots$  ... Capacitors in parallel.

## 2 Capacitors

1. Consider Fig. 1. *The sum* of all the capacitances is the total capacitance. Why do you think it works this way?

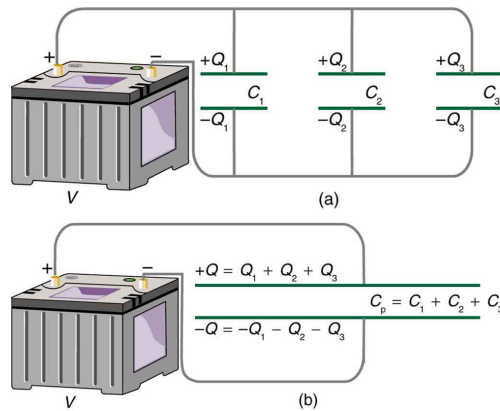


Figure 1: The relationship between potential energy and voltage.

2. Suppose  $C_1$  is 20 nF,  $C_2$  is 20 nF, and the total capacitance is 100 nF. What is the capacitance of  $C_3$ ?
3. Suppose the total charge stored is 500 nC. At what voltage is the charge being stored?
4. Suppose a different system stores the same charge at half the voltage. What is true of the capacitance?
  - A: It has half the capacitance
  - B: It is the same capacitance
  - C: It is double the capacitance
  - D: It has zero capacitance