

RC Circuit Analysis

Jordan C. Hanson

February 4, 2026

Abstract

An RC circuit is any simply connected circuit with resistance and capacitance. If a battery with emf $\mathcal{E}$ is connected to a resistor R and capacitor C , the voltage on the capacitor V_C will charge until $V_C \rightarrow \mathcal{E}$. If the capacitor is connected to a load R_L , then the load will receive current until $V_C \rightarrow 0$.

1 Required Equipment

Check that your lab table has the following items: (1) a DC power supply, (2) a digital voltmeter, (3) a 1 Farad capacitor, (4) a 470 Ohm resistor, blue (5) a light bulb, (6) an electric switch, (7) one black wire with alligator clips, (8) and three red wires with alligator clips. You will also need the stopwatch on your smartphone, or the stopwatch on the clock application on the desktop PC at your lab table.

2 Setup

Plug in the DC power supply, and click the power switch. Turn the current knob until the notch is at the top. This knob controls the maximum current the unit supplies, and is called the *current limit*. Turn the voltage knob until the digital display reads 5.0 V. Use the digital voltmeter to verify the voltage is set to 5.0 V by touching the red voltmeter lead to the red output of the supply, and the black voltmeter lead to the black output of the supply. Turn the voltmeter knob to the “200 V” setting. This gives a precision of 0.1 V. The next lowest setting is “2 V,” which gives more precision for voltages below 2 V.

Move the electric switch to the open position, with the handle straight upward. Turn off the DC power supply without changing the knobs. Connect a red wire from the red DC supply output to one of the outer switch screws. If the switch is tilted left, it connects the left screw to the center screw. If tilted right, it connects the center and right screws. Connect a red wire between the center screw and one end of the resistor. Check that the resistor has a value of 470Ω using the voltmeter. You must turn the voltmeter center knob to the Ω -section and obtain a few digits of precision. Connect the third red wire to the free end of the resistor and the capacitor post that does not have the black stripes.

Connect the black wire to the free end of the capacitor with the black stripes and the black output of the DC power supply. Prepare the digital voltmeter to measure voltages less than 2V. Use a stopwatch on your smartphone, or on the desktop PC at your table, to record the time in seconds. We are going to turn on the DC power supply and close the switch. Once the switch is closed, a small current will begin to flow into the capacitor.

3 Graphing the Capacitor Voltage, V_C

Let $\mathcal{E} = 5 \text{ V}$, $\tau = RC$, $R = 470\Omega$, and $C = 1\text{F}$. What is the expected value of τ , in seconds? The charging capacitor voltage is expected to follow

$$V_C(t) = \mathcal{E} (1 - e^{-t/\tau}) \quad (1)$$

Create a graph of Eq. 1 in the space below. Draw a straight, horizontal axis for time, and a straight, vertical axis for V_C . Label your axis with Volts and seconds. Plot Eq. 1 using a graphing calculator, web browser, or Excel. Evaluate 10 points from Eq. 1 and add these points to your graph so that you can draw Eq. 1 accurately.

Graph:

4 Measuring V_C

Close the switch and start the stopwatch simultaneously. Use the digital voltmeter to measure V_C every 30 seconds for about two time constants, or until V_C seems fully charged. Add each point to the graph in Sec. 3, and an Excel or Google Sheets spreadsheet using the desktop PC or your own device. Time should be the first column, and V_C should be the second column. Decide upon a reasonable voltage precision, given your voltmeter properties, and record a voltage error in a third column. Let $V_{\text{meas},i}$ represent the i -th piece of data in your second column, and $V_{\text{exp},i}$ represent the i -th value given by Eq. 1 for the time in your first column. Finally, let σ_i represent the assumed error in $V_{\text{meas},i}$. In a fourth column, compute the following quantity:

$$\chi_i^2 = \frac{(V_{\text{meas},i} - V_{\text{exp},i})^2}{\sigma_i^2} \quad (2)$$

5 Comparing Theory and Experimental Data

Go to the Curve-Fitting PhET simulation:

<https://phet.colorado.edu/en/simulations/curve-fitting>

and explore the controls. We can drag and drop data points onto an x-y plane, and the points have adjustable errors. Clicking “Curve” in the right-hand box runs an algorithm to fit a predictive equation to the data. The curve can be linear, with two parameters (slope and offset). The curve

can be quadratic or cubic, with three or four tunable parameters, respectively. Obtain a linear best fit to a roughly linear data set, and then click “Adjustable fit.”

The adjustable fit function allows you to tune the slope and offset independently. Notice what happens to the χ^2 statistic (left bar) as you tune. When the fit is good, we observe that $X^2 \gtrsim 1$. When a fit is bad, $X^2 \rightarrow \infty$. Notice that if you obtain a best fit, and then choose quadratic or cubic, χ^2 can be reduced by adding more parameters. This is known as *over-fitting*. Theoretically, we could choose a polynomial with a large number of parameters that would match *any* data-set. The idea is to fit the data with as few parameters as possible. Click the blue information button beneath χ^2 in the left bar to reveal Eq. 3 (below), called the *reduced chi-square* statistic.

The reduced chi-square statistic is used to assess the goodness-of-fit provided by a model for a data set. This test is used for continuous data, not categorical data. The latter arises in other branches of physical and social sciences, and it should be treated as a separate idea. Our χ^2 should approach a theoretical χ^2 , provided we have enough data points.

Let $f = 2$ to represent the number of free parameters in Eq. 1, $\mathcal{E}$ and τ . Let N be the total number of measurements $V_{C,\text{meas}}$. The *degrees of freedom* is $N - f$, the number of independent data points our model can explain. Compute the reduced chi-square by summing the values given by Eq. 2 and dividing by $N - f$:

$$\chi^2 = \frac{1}{N - f} \sum_{i=1}^N \chi_i^2 \quad (3)$$

Quote your χ^2 result below. Note that we are not fine-tuning $\mathcal{E}$ or τ to minimize χ^2 , because these are measured parameters in our experiment. Rather, your reduced chi-square statistic is an indication of how well Eq. 1 describes the data. If $\chi^2 \gtrsim 1$, we have a model that fits the data without overfitting it. In your own words, describe how well you observe agreement between model and data.

χ^2 _____

6 Conclusion

Once you have completed your measurements, computed χ^2 , and checked that χ^2 approaches the expected value of χ^2 (about 1), we have one final step. Use the wires to connect the bulb in series with the capacitor and resistor. What current do you predict will flow through the bulb? Do you see light from the bulb, and does it fade? What equation should describe V_C versus time?